

# Lab 05:

## HW 4

Hunjun Lee


[hunjunlee@hanyang.ac.kr](mailto:hunjunlee@hanyang.ac.kr)

# Overview

- ◆ You will upgrade your single cycle CPU into a multicycle CPU
- ◆ What to do?
  - Define additional control signals for multi-cycle architecture
  - Build an FSM to control multi-cycle execution
  - Rearchitect the datapath and finalize your design

 
# Multicycle Implementation

- ◆ You will be implementing a **up-to five-stage multicycle CPU**
- ◆ Each stage will take a single clock cycle
  - IF -> ID -> EX -> MEM -> WB
- ◆ Refer to the following FSM
  - Define your own FSM for JR and JAL, ...



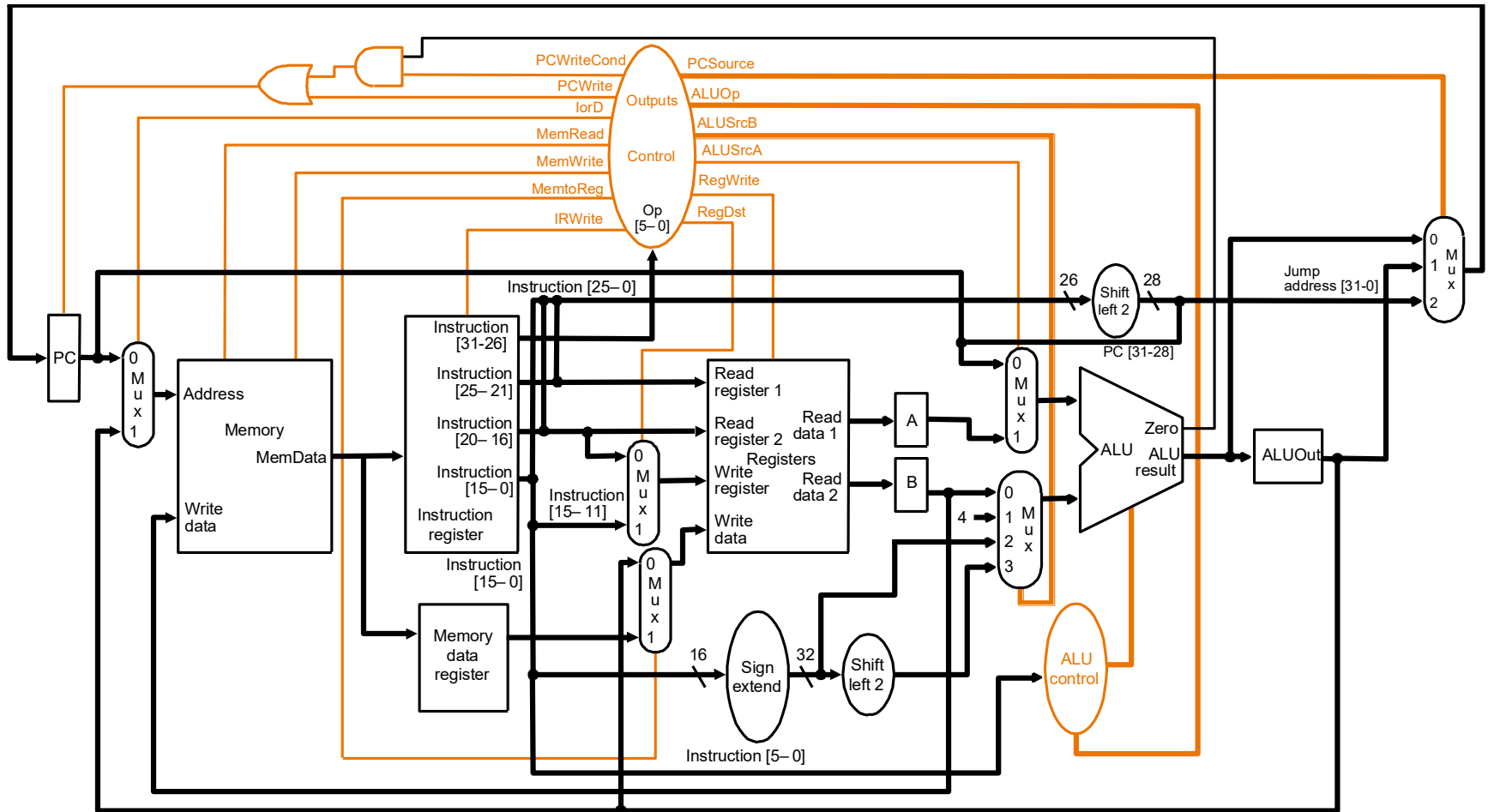
# Target CPU Microarchitecture - 1

- ◆ Implement what you learned in the class, but again you need to **support jal and jr**


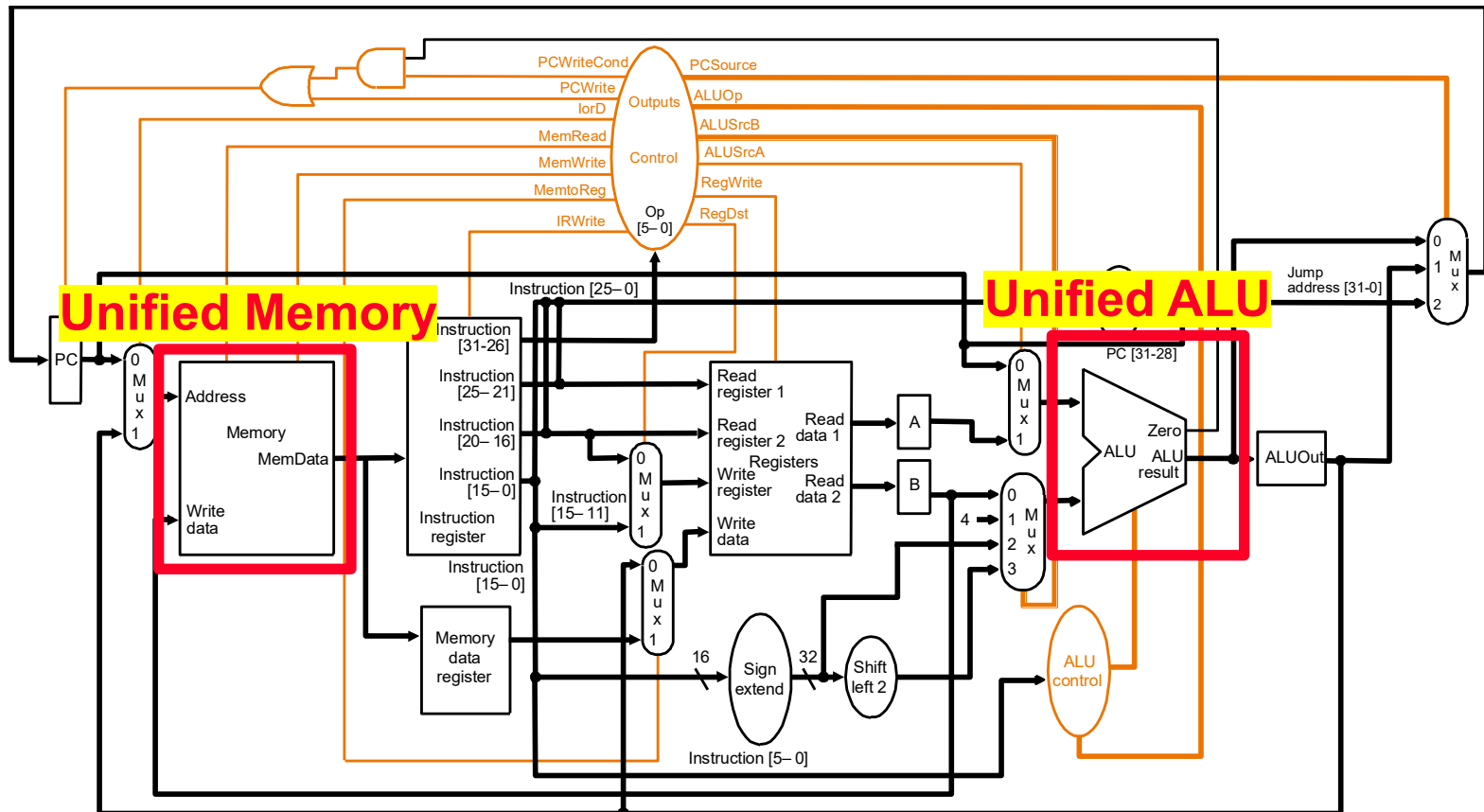
# Target CPU Microarchitecture - 2

- ◆ Also, you should **share resources** among different computation stages (penalty if you do not or only partially share resources)



# Assignment

## ◆ Files:

- `global.h + GLOBAL.v` (HW3)
  - Include constant values (opcode, funct ...)
  - You may change it to define states
- `ALU.cpp/h + ALU.v` (HW1)
- `RF.cpp/h + RF.v` (HW2)
- `MEM.cpp/h + MEM.v` (Provided)
  - Modify the memory module (make it share a single port)
- `CTRL.cpp/h + CTRL.v` (Modify HW3)
  - A controller to determine control signals
- `CPU.cpp/h + CPU.v` (Modify HW3)
  - The top module to combine these modules
- `main.cpp + CPU_tb.v` (HW3)
  - I gave you the test files for HW3 (Use it)

# Unified Memory Module Implementation

- ◆ Now, your memory module should integrate
  - instruction addr w/ memory addr
  - read data w/ inst

```
void MEM::memAccess(uint32_t addr, uint32_t *read_data, uint32_t *write_data) {
    // Do not change the status is not intended to read or write
    if (!MemRead && !MemWrite) return;
    // Check alignment + data memory capacity
    if (addr % 4 == 0) {
        addr = addr >> 2;
        if (addr >= DATAEND) {
            status = MEM_OVERFLOW; return;
        }
    }
    else {
        status = MEM_UNALIGNED; return;
    }

    if (MemWrite)
        memory[addr] = write_data;
    else if (MemRead)
        *read_data = memory[addr];
}
```

```
`timescale 1ns / 1ps

module MEM(
    input          clk,
    input          rst,

    input [31:0]   mem_addr,
    input          MemWrite,
    input [31:0]   mem_write_data,
    output reg [31:0] mem_read_data
);

    reg [31:0] memory [0:8191];

    initial begin
        $readmemh("initial_mem.mem", memory);
    end

    always @(*) begin
        mem_read_data = memory[(mem_addr >> 2)];
    end

    always @(posedge clk) begin
        if (!rst)
            if (MemWrite)
                memory[(mem_addr >> 2)] <= mem_write_data;
    end

endmodule
```

# Submission

- ◆ Submission (Zip all the files)
  - For a two-people team: lab4\_student\_id1\_student\_id2.zip
  - For a one-person team: lab4\_student\_id.zip
    - You must follow the format (-10% for wrong file format)
    - Example:
      - lab4\_2020102030.zip
      - lab4\_2020102030\_2022103040.zip
  - The zip file should contain:
    - every cpp/h/v files
    - lab4\_report.pdf



# Submission

- ◆ You need to write a 4+-page report
  - Explain the overall structure and how you implemented each program
  - What's your FSM to implement JAL and JR instruction?
  - Draw the hardware modules if needed ...
  - How did you implement JAL / JR instruction and modified the uarchitecture?
- ◆ Due: Fri. May 9<sup>th</sup>
  - 1 week delay: -20%
  - 2 week delay: -50%
  - Further delay: 0 point
- ◆ You can submit HW3 by May 9<sup>th</sup> with only 20% deduction